TED (10) - 3059

(REVISION - 2010)

https://www.gptcthirurangadi.in

Reg. No. ______Signature ______

DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/ MANAGEMENT/COMMERCIAL PRACTICE — OCTOBER, 2018

DIGITAL ELECTRONICS

[Time: 3 hours

(Maximum marks : 100)

PART - A

(Maximum marks : 10)

Marks

I Answer all questions in one or two sentences. Each question carries 2 marks.

- 1. Define weighted code with example.
- 2. Define fan-in in logic gates.
- 3. Define propagation delay in logic family.
- 4. Define sequential circuits.
- 5. Write the type of ADCs.

PART - B

(Maximum marks : 30)

- II Answer any five of the following questions. Each question carries 6 marks.
 - 1. State and explain De-Morgan's theorems.
 - 2. Simplify the Boolean expression.

 $\mathbf{Y} = \mathbf{T}(0,1,3,5,6,7,10,14,15).$

- 3. Explain the race around condition.
- 4. Explain the working of full adder circuit using logic gates and truth table.
- 5. Explain the working of T flip-flop circuit with truth table.
- 6. Compare SDRAM and EDORAM.
- 7. Define accuracy, resolution and monotonicity.

 $(5 \times 6 = 30)$

 $(5 \times 2 = 10)$

https://www.gptcthirurangadi.in



2

PART - C

(Maximum marks : 60)

(Answer one full question from each unit. Each full question carries 15 marks.)

Unit — I

III (a) Do the following operation :

- (i) $(284)_{10}$ to Binary.
- (ii) 010101-101010 (using 2's complement)
- (iii) Convert $(6A2.3)_{16}$ into decimal.
- (iv) 110101×110 .
- (b) What is mean by binary codes? Give the list of binary codes.

Or

- IV (a) Draw the basic gates using NOR gates only.
 - (b) Simplify using K'map and draw the logic circuit diagram.

 $Y = ABCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C + AB$

V (a) Explain the working of
$$8 \times 1$$
 Multiplexer with diagram.

(b) Explain the circuit diagram of TTL inverter.

Or

- VI (a) Explain about BCD to seven segment decoder with diagram.
 - (b) Compare positive and negative logics.

UNIT --- III

- VII (a) Explain about JK flip-flop with diagram and truth table.
 - (b) Explain the working of 3 bit ring counter.

OR

 VIII
 (a) Explain the working of 3-bit Asynchronous ripple counter.
 9

 (b) Explain the working of right shift register with diagram.
 6

 UNIT — IV
 IX

 IX
 Draw and explain the working of R-2R ladder network DAC.
 15

Or

X (a) Explain the working of ROM with diagram.

(b) Compare Flash ROM and NVRAM.

Marks

8

7

6

9

8

7

9

6

9

6

8

7