



TED (15/19) 2041
(Revision – 2015/19)

A22 –04435

<https://www.gptchirurangadi.in>

Reg. No.....
Signature

**DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/
MANAGEMENT/COMMERCIAL PRACTICE, APRIL – 2022**

BASIC ELECTRONICS

[Maximum Marks: 100]

[Time: 3 Hours]

(PART-A)

(Answer *all* questions in one or two sentences. Each question carries 2 marks)

- I. 1. Compare active and passive components.
2. Define Resistance and write its unit.
3. Explain doping.
4. List any two types of filter circuits.
5. Draw the symbol of PNP & NPN transistors. (5 x 2 = 10)

(PART-B)

(Answer *any five* of the following questions. Each question carries 6 marks)


- II. 1. Define Self and Mutual inductance.
2. Describe Intrinsic & Extrinsic semiconductors.
3. Distinguish between Zener breakdown & Avalanche breakdown.
4. Explain the terms TUF, Rectification efficiency and Ripple factor.
5. Summarize the working principle of a Half wave voltage doubler circuit.
6. State the effect of temperature in leakage current.
7. Discuss about the operation of an NPN transistor. (5 x 6 = 30)

(PART-C)

(Answer *one* full question from each Unit. Each full question carries 15 marks)

UNIT – I

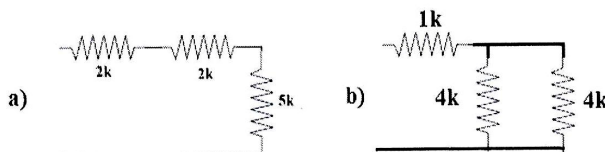- III. (a) Explain the working principle of transformers and list any three applications. (9)
(b) Find the effective resistance of given circuits. (6)





OR

- IV. (a) Classify different capacitors. (7)
(b) Briefly elaborate the color coding of Resistors. (8)

UNIT – II

- V. (a) With the help of V-I characteristics, explain the principle of operation of diode. (9)
(b) With the help of energy band diagram distinguish between insulators, conductors and semiconductors. (6)

OR

- VI. (a) Explain the working of Zener diode as a voltage regulator. (9)
(b) Elaborate the working principle of Tunnel Diode with its V-I characteristics. (6)

UNIT- III

- VII. (a) Compare Half wave, Full wave & Bridge Rectifiers. (9)
(b) Explain the working of a positive shunt clipper. (6)

OR

- VIII. (a) Compute Average and RMS values of voltage and current of half wave rectifier. (9)
(b) Explain the working of a π section filter. (6)

UNIT - IV

- IX. (a) Explain input and output characteristics of BJT in CB configurations. (9)
(b) Derive relation between α , β , γ . (6)

OR

- X. (a) Compare CB, CE & CC configurations. (9)
(b) Define input & Output resistance in CE configuration. (6)
